

# Digital Logic Structures

Joannah Nanjekye

July 10, 2024

# Outline

Boolean Algebra

The Transistor

Logic Gates

Combinational Circuits

# Boolean Algebra


- ▶ A mathematical discipline used in the analysis and design of digital circuits
- ▶ It uses logical variables and operations
- ▶ Variables:
  - ▶ 1 (TRUE)
  - ▶ 0 (FALSE)
- ▶ Operations:
  - ▶  $A \text{ AND } B = A \cdot B$
  - ▶  $A \text{ OR } B = A + B$
  - ▶  $\text{NOT } A = \bar{A}$

# Identities of Boolean Algebra

<b>Basic Postulates</b>		
$A \cdot B = B \cdot A$	$A + B = B + A$	Commutative Laws
$A \cdot (B + C) = (A \cdot B) + (A \cdot C)$	$A + (B \cdot C) = (A + B) \cdot (A + C)$	Distributive Laws
$1 \cdot A = A$	$0 + A = A$	Identity Elements
$A \cdot \bar{A} = 0$	$A + \bar{A} = 1$	Inverse Elements
<b>Other Identities</b>		
$0 \cdot A = 0$	$1 + A = 1$	
$A \cdot A = A$	$A + A = A$	
$A \cdot (B \cdot C) = (A \cdot B) \cdot C$	$A + (B + C) = (A + B) + C$	Associative Laws
$\overline{A \cdot B} = \bar{A} + \bar{B}$	$\overline{A + B} = \bar{A} \cdot \bar{B}$	DeMorgan's Theorem
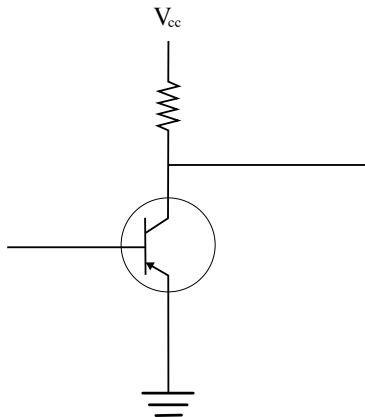
# The Transistor

A transistor is a semiconductor device used to amplify and switch electronic signals



# Logic Gates

Electronic circuits that produce output signals that are Boolean operations on their input signals


When the gate input changes, the output is instant unless a gate delay occurs as a result of signal propagation time

Digital logic uses the following gates:

- ▶ AND
- ▶ OR
- ▶ NOT
- ▶ NAND
- ▶ NOR
- ▶ XOR


# The NOT Gate (inverter)

$A$	$\bar{A}$
0	1
1	0

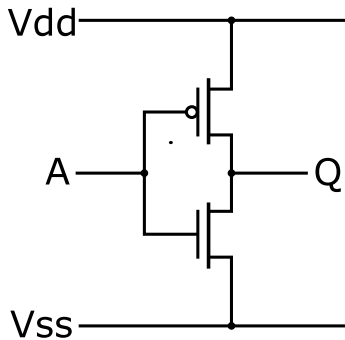

# The OR Gate


$A$	$B$	$A + B$
0	0	0
0	1	1
1	0	1
1	1	1

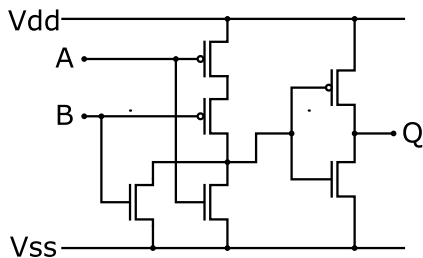




# The XOR Gate

$A$	$B$	$A \oplus B$
0	0	0
0	1	1
1	0	1
1	1	0

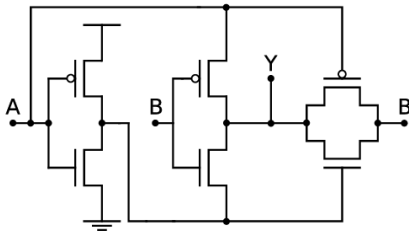

# The NOR Gate

$A$	$B$	$\overline{A+B}$
0	0	1
0	1	0
1	0	0
1	1	0

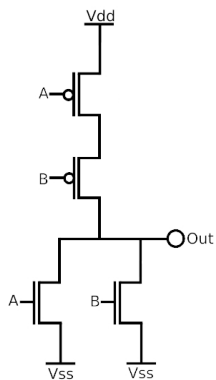


# The AND Gate

<i>A</i>	<i>B</i>	<i>AB</i>
0	0	0
0	1	0
1	0	0
1	1	1

How would you construct an AND gate?






# The NAND gate

$A$	$B$	$\overline{AB}$
0	0	1
0	1	1
1	0	1
1	1	0

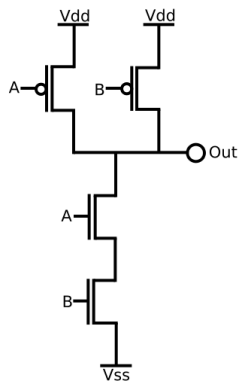
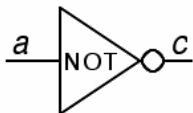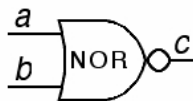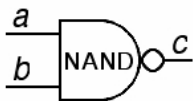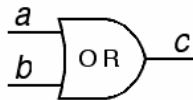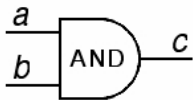
## Logic Gate Symbols

**Assert** a signal is to cause a signal line transition from its logically false (0) state to its logically true (1) state



# DeMorgan's Law

$$AB = \overline{\overline{A} + \overline{B}}$$

$$A + B = \overline{\overline{A} \cdot \overline{B}}$$

Show the relationship between AND and OR gates.  
AND, OR, NAND, and NOR gates may have more than two inputs.

# Complete Sets of gates



Any Boolean function can be implemented using a subset of gates

We need to identify a functionally complete set of gates

The following sets of gates are functionally complete



- ▶ AND, OR, NOT
- ▶ AND, NOT
- ▶ OR, NOT
- ▶ NAND
- ▶ NOR

# Using NAND Gates

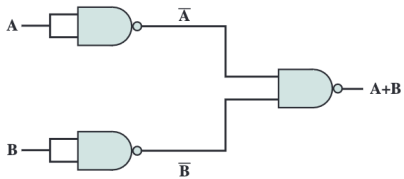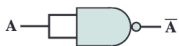



# Using NOR Gates

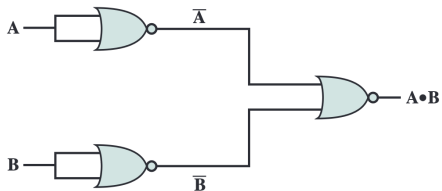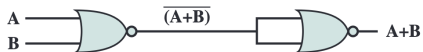

# Combinational Circuits

- ▶ An interconnected set of gates
- ▶ The output at any time is a function only of the input at that time
- ▶ The output is determined by the input
- ▶ Examples
  - ▶ Adder
  - ▶ Decoder
  - ▶ MUX

# Design of Combinational Circuits

- ▶ Problem statement
- ▶ Formal specification
  - ▶ Truth table
  - ▶ Boolean equation
  - ▶ Graphical symbols: hardware description language (eg VHDL)
- ▶ Minimize
- ▶ Implementation

# Design of Combinational Circuits

## Example

A car key alert should be turned on under the following circumstances:

- ▶ The key is in and the door is open;
- ▶ The key is not in and the light is on.

The system has three inputs:

- ▶  $L$  - the lights are on
- ▶  $K$  - the key is in
- ▶  $D$  - the door is open

The system has one output:

- ▶  $B$  - the buzzer will be activated

# Description to Truth Table

From the description we can obtain the truth table

<i>L</i>	<i>K</i>	<i>D</i>	<i>B</i>
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	0
1	1	1	1

# Sum of Products

The Sum of Products (SOP) has one term for each 1 in the output

<i>L</i>	<i>K</i>	<i>D</i>	<i>B</i>
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	0
1	1	1	1

$$B = \bar{L}KD + L\bar{K}\bar{D} + L\bar{K}D + LKD$$

# Product of Sums

The Product of Sums (POS) has one term for each 0 in the output

$L$	$K$	$D$	$B$
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	0
1	1	1	1

$$(\overline{L} + \overline{K} + \overline{D}) \cdot (\overline{L} + \overline{K} + D) \cdot (\overline{L} + K + \overline{D}) \cdot (L + K + \overline{D})$$

# Definitions

## Definition (Literal)

A variable  $X$  has two **literals**  $X$  and  $\bar{X}$ .

## Definition (Product term)

A logical product where each variable is represented by at most one literal is a **product** or a **product term** or a **term**. A term can be a single literal.

## Definition (Sum-of-products)

A logical sum of product terms forms a sum-of-products expression (SOP).



# Definitions

## Definition (Minterm)

A **minterm** is a logical product of  $n$  literals where each variable occurs as exactly one literal

## Definition (Canonical SOP)

A **canonical SOP** is a logical sum of minterms, where all minterms are different. Also called canonical disjunctive form or minterm expansion.

# Problem

- ▶ List the minterms;  
 $B(L, K, D) = \Sigma m(3, 4, 5, 7)$
- ▶ Write the canonical SOP for the car buzzer problem;  
 $B(L, K, D) = \overline{L}KD + \overline{L}\overline{K}\overline{D} + \overline{L}\overline{K}D + LKD$
- ▶ draw the circuit;
- ▶ how can it be minimized?
- ▶ show that  $\overline{L}\overline{K} + KD + LD = \overline{L}\overline{K} + KD$

# Simplification of a Boolean Expression

A Boolean function can be realized in either SOP or POS form

However we need a simpler Boolean expression that uses fewer gates:

- ▶ Algebraic simplification
- ▶ Karnaugh maps
- ▶ Quine-McCluskey tables

# Algebraic Simplification

- ▶ Involves the use of boolean algebra identities
- ▶ To reduce the Boolean expression to one with fewer elements
- ▶ Or even simple observation, for example:

$$F = \overline{A}B + B\overline{C}$$

- ▶ Can be simplified as:

$$F = B(\overline{A} + \overline{C})$$