
 


Combinational Building Blocks

Joannah Nanjehye

July 16, 2024


A Half Adder

 


- ▶ Add two bits *A* and *B*
- ▶ Output the sum *S*
- ▶ Output the carry *C*

<i>A</i>	<i>B</i>	<i>C</i>	<i>S</i>
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

A Full Adder

 


 - ▶ Add three bits A , B , and C_{in}
- ▶ Output the sum S
- ▶ Output the carry C_{out}



A	B	C_{in}	C_{out}	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

A 4-bit Adder

 

- ▶ Constructed with full adders connected in cascaded
- ▶ Carry output from each adder is connected to the carry input of the next adder in the chain
- ▶ Carry input is from the least significant bit (LSB)
- ▶ The sum output is represented by the bits s_0 - s_3

Ripple Carry Adder Delays


- ▶ An output sum and carry is determined after the carry created from the previous stages is produced
- ▶ The sum of the MSB is known after the carry signal has rippled through the adders from the LSB
- ▶ Final sum and carry bits will be valid after a considerable delay
- ▶ For an n - bit the delay is:

$$\text{Sum}_{s_{n-1}} \text{ delay} = 4n + 2$$

$$\text{Carry}_{c_n} \text{ delay} = 4n + 3$$

Carry Lookahead Adder (CLA)

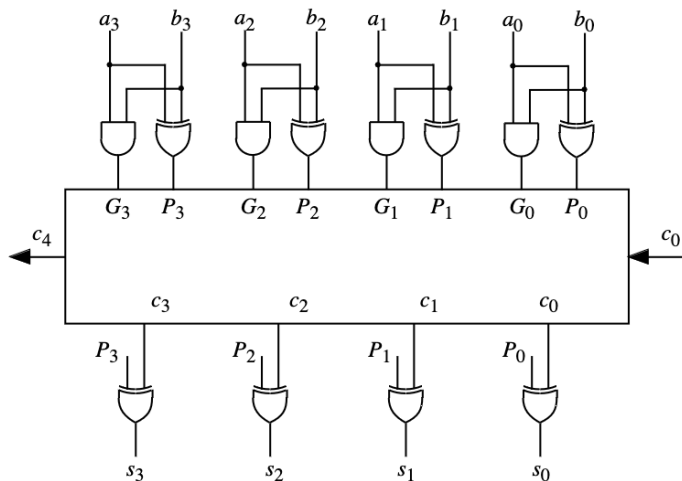- ▶ Calculate the carry signals in advance, based on the input signals



Carry lookahead adder (CLA)

- ▶ Assumes a carry signal can be generated in two cases:
 - ▶ When both bits are 1
 - ▶ When one of the two bits is 1 and the carry-in is 1
- ▶ We can therefore write the equations:

$$C_{i+1} = G_i + P_i \cdot C_i$$

$$S_i = P_i \oplus C_i$$

- ▶ Where:

$$G_i = a_i \cdot b_i$$

$$P_i = a_i \oplus b_i$$

Advantages and Disadvantages of Carry Look-Ahead Adder

Advantages:


- ▶ The propagation delay is reduced
- ▶ It provides the fastest addition logic

Disadvantages:

- ▶ The Carry Look-ahead adder circuit gets complicated as the number of variables increase
- ▶ The circuit is costlier as it involves more number of hardware


Decoders

 - ▶ A decoder selects one of 2^n outputs according to an encoded input (n bits)
- ▶ Only one of the outputs is asserted based on the combination of inputs present
- ▶ When the decoder is enabled
- ▶ When an “enable” input, enable = 0 then all outputs are 0



2 to 4 Decoder

 The outputs of the decoder are the min terms of n input variables lines, when it is enabled



E	A	B	Y_0	Y_1	Y_2	Y_3
0	x	x	0	0	0	0
1	0	0	0	0	0	1
1	0	1	0	0	1	0
1	1	0	0	1	0	0
1	1	1	1	0	0	0



$$Y_3 = E \cdot A \cdot B$$

$$Y_2 = E \cdot A \cdot \bar{B}$$

$$Y_1 = E \cdot \bar{A} \cdot B$$

$$Y_0 = E \cdot \bar{A} \cdot \bar{B}$$


2 to 4 Decoder

  

Constructing Higher Order Decoders




of decoders = m_2/m_1

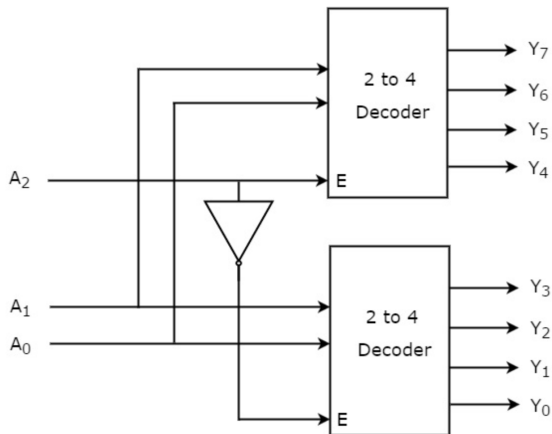of 2 to 4 decoders = 8/2 for a 3 to 8 decoder




Encoders

   - ▶ A encoder is the inverse of a decoder
- ▶ It is not used frequently as decoders




4 to 2 Encoder

HIGHEST	INPUTS		LOWEST	OUTPUT	
D3	D2	D1	D0	Y0	Y1
0	0	0	0	X	X
0	0	0	1	0	0
0	0	1	X	0	1
0	1	X	X	1	0
1	X	X	X	1	1

 


Multiplexer

 - ▶ A multiplexer or mux is a device that selects one of several input signals and forwards the selected input into a single line
- ▶ A multiplexer of 2^n inputs has n select lines




Multiplexer

 


S2	S1	F
0	0	D0
0	1	D1
1	0	D2
1	1	D3

Arithmetic and Logic Unit (ALU)

 

Constructing an ALU

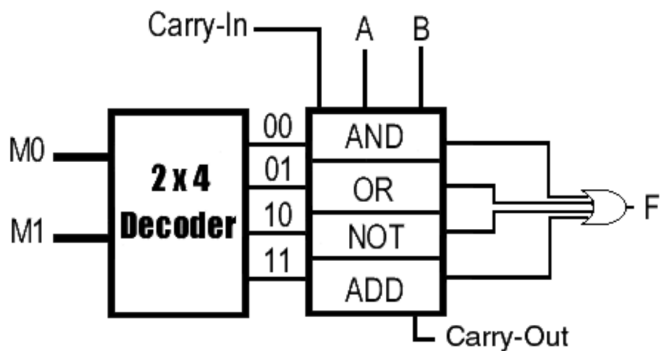

Memory in Combinational Circuits

- ▶ These circuits can also have memory
- ▶ The kind is called read-only memory (ROM)
- ▶ ROM is permanent and created during fabrication
- ▶ Outputs are a function of the present inputs
- ▶ Can be implemented with a decoder and a set of OR gates

ROM

Input				Output			
X ₁	X ₂	X ₃	X ₄	Z ₁	Z ₂	Z ₃	Z ₄
0	0	0	0	0	0	0	0
0	0	0	1	0	0	0	1
0	0	1	0	0	0	1	1
0	0	1	1	0	0	1	0
0	1	0	0	0	1	1	0
0	1	0	1	0	1	1	1
0	1	1	0	0	1	0	1
0	1	1	1	0	1	0	0
1	0	0	0	1	1	0	0
1	0	0	1	1	1	0	1
1	0	1	0	1	1	1	1
1	0	1	1	1	1	1	0
1	1	0	0	1	0	1	0
1	1	0	1	1	0	1	1
1	1	1	0	1	0	0	1
1	1	1	1	1	0	0	0

ROM

