

Sequential Circuits

Joannah Nanjehye


July 17, 2024

Sequential Circuits

The current output of a sequential circuit depends on the current input and the current state of that circuit


The circuit contains storage elements

 It is basically a combinational circuit with a memory component



Flip-Flops

 - ▶ A form of sequential circuit
- ▶ Characteristics of flip-flops:
 - ▶ It is a bistable device, exists in two states
 - ▶ Has two outputs, that are complements of each other
 - ▶ Constructed with NAND or NOR gates



(a) Circuit

S	R	Q _a	Q _b
0	0	0/1	1/0 (no change)
0	1	0	1
1	0	1	0
1	1	0	0


(b) Truth table

SR Latch

R	S	Q_{n+1}	\overline{Q}_{n+1}	
0	0	Q_n	\overline{Q}_n	previous state
0	1	1	0	set Q to 1
1	0	0	1	reset Q to 0
1	1	0	0	forbidden

Clocked SR flip-flop

 - ▶ In the basic SR latch, the state changes only on input change
- ▶ For more control we need to add a clock to the latch to change state at particular times
- ▶ Problem with the SR latch: a spike in S or R will set/reset Q
- ▶ Solution: only allow S or R to change when the clock is low




(a) Circuit

Clk	S	R	$Q(t+1)$
0	x	x	$Q(t)$ (no change)
1	0	0	$Q(t)$ (no change)
1	0	1	0
1	1	0	1
1	1	1	x

 (b) Characteristic table

Gated D latch


- ▶ The condition $R = 1, S = 1$ must be avoided (allow one input)
- ▶ Has one input instead of two
- ▶ Capture the data when the clock is high
- ▶ As long as the E is high the output changes according to the input



(a) Circuit

Clk	D	$Q(t+1)$
0	x	$Q(t)$
1	0	0
1	1	1


(b) Characteristic table

 

 (c) Graphical symbol


Edge Triggering

- ▶ Design storage elements where the output changes only when the clock changes
- ▶ These circuits are called edge triggered
- ▶ Propagation delay for a D latch:
 - ▶ Stores the value of D input at the time clock goes from 1 to 0
 - ▶ Operates properly if input is stable (not changing) at the time clk goes from 1 to 0




Positive-edge-triggered D flip-flop

 - ▶ The output should only change once during a clock cycle
- ▶ Change on the edge of a cycle
- ▶ This can be accomplished as follows (master-slave)
- ▶ Master, changes its state when $\text{clk}=1$
- ▶ Slave, changes its state when $\text{clk}=0$




(a) Circuit

 

 (b) Graphical symbol

Positive-edge-triggered T flip-flop


- ▶ The output “flips” if $T = 1$; no change if $T = 0$



(a) Circuit

T	$Q(t+1)$
0	$Q(t)$
1	$\bar{Q}(t)$


(b) Truth table

 

 (c) Graphical symbol


Positive-edge-triggered JK flip-flop

- ▶ $J=S$ and $K=R$ and behaves like a SR flip-flop
- ▶ Except all states are valid
- ▶ This is achieved by toggling the output



J	K	Q(t+1)
0	0	Q(t)
0	1	0
1	0	1
1	1	$\bar{Q}(t)$


(b) Truth table

 

Registers

- ▶ A number of flip-flops used to store bits of data i.e, n flip-flops store n bits information
- ▶ Two kinds of registers:
 - ▶ **Shift Registers:** accept and/or transfers data serially
 - ▶ **Parallel Registers:** has a set of 1-bit memories that can be read or written simultaneously

Shift Register

 


(a) Circuit

	In	Q ₁	Q ₂	Q ₃	Q ₄ = Out
t_0	1	0	0	0	0
t_1	0	1	0	0	0
t_2	1	0	1	0	0
t_3	1	1	0	1	0
t_4	1	1	1	0	1
t_5	0	1	1	1	0
t_6	0	0	1	1	1
t_7	0	0	0	1	1


(b) A sample sequence

Parallel Register

 

Counters

 
- ▶ Circuits that can increment or decrement a count by 1
- ▶ Can be built with T and D flip-flops
- ▶ Counters can be:
 - ▶ asynchronous
 - ▶ synchronous



 (a) Circuit

Asynchronous Counters


- ▶ In our example a counter has three flip-flops but can have more latches
- ▶ The first flip-flop is the only one that is clocked (attached to the clock)
- ▶ The other flip-flops experience a propagation delay that affects their response



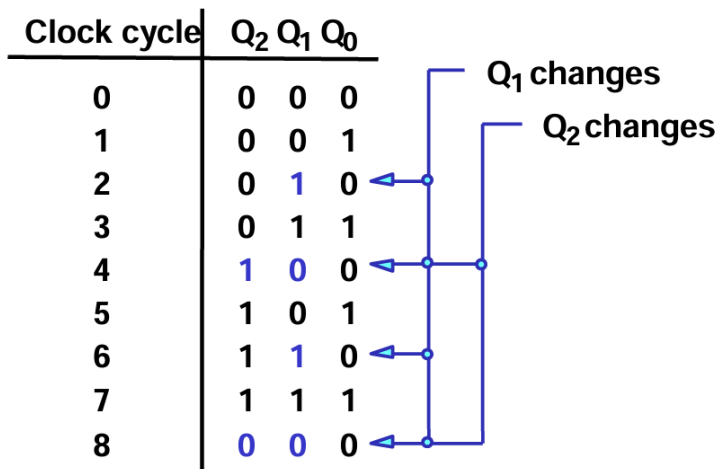(a) Circuit


Synchronous Counters

- ▶ Solves the challenges for asynchronous counters
- ▶ By clocking all the flip-flops at once



Synchronous Counters

 
- ▶ Q0 is triggered on each clock cycle
- ▶ Q1 is triggered when Q0=1
- ▶ Q2 is triggered when Q1=1 and Q0=1



 (a) Circuit

Synchronous Counters


- ▶ $T_0 = 1$
- ▶ $T_1 = Q_0$
- ▶ $T_2 = Q_0 Q_1$
- ▶ $T_3 = Q_0 Q_1 Q_2$



 (a) Circuit

Ring Counter

- ▶ Counters usually have state in flip-flops
- ▶ For ring counters, the output of the last flip-flop is connected as an input to the first flip-flop
- ▶ The non-complemented output is the one that is connected back to the input



(a) An n -bit ring counter


Ring Counter

- ▶ Can be made of D-flip flops or JK-flip flop
- ▶ Has Mod = n , n is the number of bits
- ▶ That is 4-bit ring counter has 4 states
- ▶ Only 4 of the 15 states are utilized

States	Q_A	Q_B	Q_C	Q_D
1	1	0	0	0
2	0	1	0	0
3	0	0	1	0
4	0	0	0	1

Johnson Counter

 - ▶ Twisted Ring counter
- ▶ Complemented output of the flip-flop is connected with the input of the first flip-flop
- ▶ Can also be built with D-flip flops or JK-flip flops



Johnson Counter

- ▶ Has Mod = $2n$, n is the bit size of the counter
- ▶ It therefore counts to a sequence of length $2n$
- ▶ Utilizes the maximum number of states

States	Q_A	Q_B	Q_C	Q_D
1	0	0	0	0
2	1	0	0	0
3	1	1	0	0
4	1	1	1	0
5	1	1	1	1
6	0	1	1	1
7	0	0	1	1
8	0	0	0	1

References

- ▶ <https://www.ece.mcmaster.ca/~xwu/2di4/chapter7.pdf>