

# Designing Sequential Circuits

Joannah Nanjehye

July 17, 2024


# Steps in Designing Sequential Circuits

1. Create a state table and/or state diagram
2. Create binary-code for the state table and/or state diagram
3. Choose a type of flip-flop
4. Add columns to the state table that show the input required for each flip flop, to effect each required transition
5. Simplify each flip-flop input(s)
6. Draw the circuit

# Example

Design a counter that has an *Enable* input. When *Enable* = 1 it increments through the sequence 0,1,2,3,0,1,... with each clock tick. *Enable* = 0 causes the counter to remain in its current state.

# 1. State Diagram

 

# 1. State Table

	<i>Enable = 0</i>	<i>Enable = 1</i>
Current	Next	Next
<i>n</i>	<i>n</i>	<i>n</i>
0	0	1
1	1	2
2	2	3
3	3	0

## 2. Binary Code for the State Table

$N$  states required  $\log_2 N$  bits

E.g 4 states = 2 bits

Current		$Enable = 0$		$Enable = 1$	
		Next		Next	
$n_1$	$n_0$	$n_1$	$n_0$	$n_1$	$n_0$
0	0	0	0	0	1
0	1	0	1	1	0
1	0	1	0	1	1
1	1	1	1	0	0

### 3. Choose a Flip-flop

- ▶ Any flip-flop can be used
- ▶ If in doubt use J-K flip-flops for their general use cases
- ▶ In this example we will use the JK flip-flop

## 4. Add Columns for Flip-flop Inputs

- Consult the excitation tables for the chosen flip flop

Current		<i>Enable = 0</i>						<i>Enable = 1</i>					
		Next						Next					
$n_1$	$n_0$	$n_1$	$n_0$	$J_1$	$K_1$	$J_0$	$K_0$	$n_1$	$n_0$	$J_1$	$K_1$	$J_0$	$K_0$
0	0	0	0	0	$X$	0	$X$	0	1	0	$X$	1	$X$
0	1	0	1	0	$X$	$X$	0	1	0	1	$X$	$X$	1
1	0	1	0	$X$	0	0	$X$	1	1	$X$	0	1	$X$
1	1	1	1	$X$	0	$X$	0	0	0	$X$	1	$X$	1

$Q_n$	$Q_{n+1}$	J	K
0	0	0	$X$
1	0	$X$	1
0	1	1	$X$
1	1	$X$	0



## 5. Simplify the Flip-Flop Input(s)

- We can use Karnaugh maps

$$J_0(E, n_1, n_0)$$

	$n_1 n_0$			
	00	01	11	10
$E$ 0		X	X	
$E$ 1	1	X	X	1

$$K_0(E, n_1, n_0)$$

	$n_1 n_0$			
	00	01	11	10
$E$ 0	X			X
$E$ 1	X	1	1	X

$$J_1(E, n_1, n_0)$$

	$n_1 n_0$			
	00	01	11	10
$E$ 0			X	X
$E$ 1		1	X	X

$$K_1(E, n_1, n_0)$$

	$n_1 n_0$			
	00	01	11	10
$E$ 0	X	X		
$E$ 1	X	X	1	


$$J_0(E, n_1, n_0) = E$$

$$K_0(E, n_1, n_0) = E$$


$$J_1(E, n_1, n_0) = E \cdot n_0$$

$$K_1(E, n_1, n_0) = E \cdot n_0$$

## 6. Draw the Circuit

 

# Example

 

- ▶ explain the state diagram
- ▶ what is the output given the input sequence:  
00110111100101111?
- ▶ assume it starts in state "A"

# Next State Table

$q$	$x = 0$	$x = 1$	$z$
$A$	$A$	$B$	0
$B$	$A$	$C$	0
$C$	$A$	$D$	0
$D$	$A$	$D$	1

- ▶ the information on the next state table is the same as in the FSM diagram
- ▶ Next step: state assignment
- ▶ how many bits do we need to keep track of the states?

# State Assignment

A possible state assignment

$q$	$q_1$	$q_2$
$A$	0	0
$B$	0	1
$C$	1	0
$D$	1	1

- ▶ how many state assignments are possible?
- ▶ are some better than others?

# Design Truth Table

$q$	$x$	$q_1$	$q_2$	$q_1^*$	$q_2^*$
$A$	0	0	0	0	0
$B$	0	0	1	0	0
$C$	0	1	0	0	0
$D$	0	1	1	0	0
$A$	1	0	0	0	1
$B$	1	0	1	1	0
$C$	1	1	0	1	1
$D$	1	1	1	1	1

# Design the circuit

- ▶ implement the FSM using D-FF
- ▶ Draw a Karnaugh map for  $q_1^*$  and  $q_2^*$
- ▶ Draw a Karnaugh map for the output
- ▶ find the equations
- ▶ draw the circuit
- ▶ this is known as a Moore Machine (the output depends on the current state only)

# D-FF equations

From the truth table (see 2 slides back) write the Karnaugh maps.

		$q_1 q_2$			
		00	01	11	10
$x$	0				
	1		1	1	1

$$q_1^* = xq_1 + xq_2$$



# D-FF equations

		$q_1 q_2$			
		00	01	11	10
$x$	0				
	1	1		1	1

$$q_2^* = xq_1 + x\overline{q_2}$$


# Output equation

The output depends **only** on the current state.

		$q_2$	
		0	1
$q_1$	0		
	1		1

$$F = q_1 q_2$$

## The circuit — with D-FFs

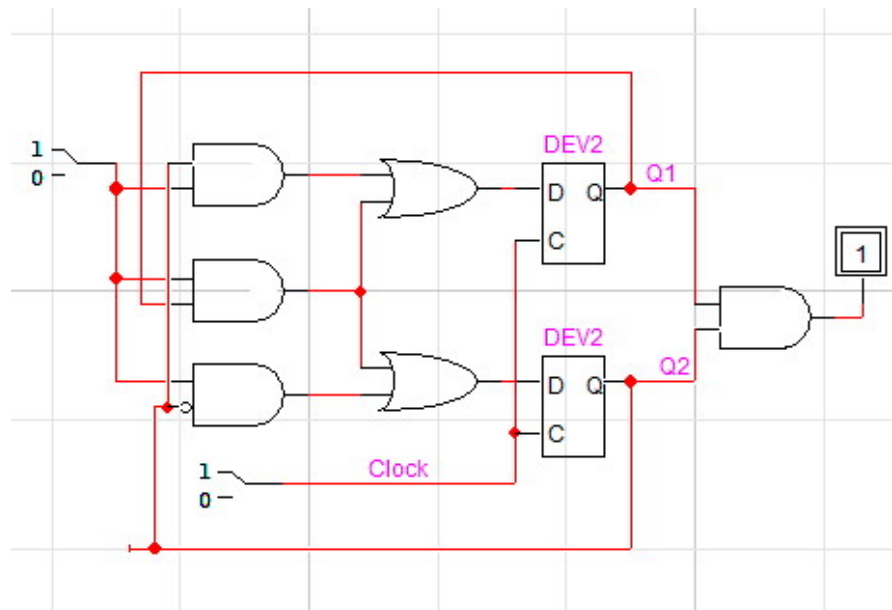

# T Flip-Flop

## Definition (T Flip-Flop)

The state is complemented if  $T = 1$ , it stays the same if  $T = 0$ .

T Flip Flop truth table

$T$	$Q_{n+1}$
0	$Q_n$
1	$\overline{Q_n}$

## Problem

*Draw the Karnaugh maps for T-FF.*

# T Flip-Flop

## D-FF

		$q_1 q_2$			
		00	01	11	10
$x$	0				
	1		1	1	1

$$q_1^* = xq_1 + xq_2$$

		$q_1 q_2$			
		00	01	11	10
$x$	0				
	1	1		1	1

$$q_2^* = xq_1 + x\overline{q_2}$$

## T-FF

		$q_1 q_2$			
		00	01	11	10
$x$	0			1	1
	1		1		

$$q_1^* = \overline{x}q_1 + x\overline{q_1}q_2$$

		$q_1 q_2$			
		00	01	11	10
$x$	0		1	1	
	1	1	1		1

$$q_2^* = \overline{x}q_2 + \overline{x_1}x_2 + x\overline{q_2}$$

# K-map Transformation Rules: from $D$ to $T$

Given a K-map for the next state variable  $x$  for a D-FF, do the following:

1. for all map entries where  $x = 0$ , transfer the values to the K map for the T-FF
2. for all map entries where  $x = 1$ , transfer the **complemented** values to the K map for the T-FF

For example, in the previous slide the first two columns for  $q_1^*$  (where  $q_1 = 0$ ) are the same, and the last two are complemented.

# JK-FF Behavioural Table

$J$	$K$	$q$	$q^*$
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	0

# JK-FF Behavioural Table

$J$	$K$	$q$	$q^*$
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	0

$J$	$K$	$q^*$
0	0	$q$
0	1	0
1	0	1
1	1	$\overline{q}$



# Example

## Problem

*Design a Moore Machine that will output a 1 iff they have been 2 ones followed by a zero and a one.*

1. draw the state diagram
2. write the next state table (include output)
3. find a state assignment
4. state table to Karnaugh maps (depends on FFs used)
5. find the equations
6. draw the circuit


# Design of an Synchronous Counter

## Problem

*Design a 4-bit counter (follow standard procedures)*

1. use D-FF
2. use T-FF
3. use JK-FF
4. compare the designs
5. can you generalize?

# Design of an Asynchronous Counter

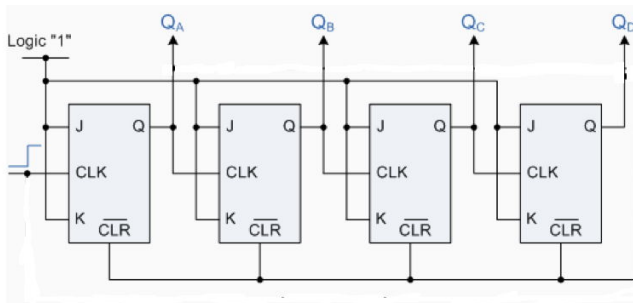

NOTE: The FFs are negative edge sensitive.

## Problem

*Modify the counter to count 0, 1, ..., 8, 9, 0, 1, ...*

# References

- ▶ <https://bob.cs.sonoma.edu/IntroCompOrg-RPi/sec-seqdes.html>
- ▶ <https://www.allaboutelectronics.org/jk-flip-flop-explained-race-around-condition-in-jk-flip-flop-jk-flip-flop-truth-table-excitation-table-and-timing-diagram/>